

IC220: HW 4


Due: 13 Feb 2019

Full Name: _____ Alpha: _____


Circle Your Section: Aviv/1001 Aviv/2001 Aviv/4001 Choi/5001 Missler/5002

Preliminary: Carefully do the assigned reading for Chapter 2 (2.1-2.3,2.5-2.10,2.12)

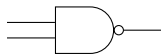1. **[5 points]** Complete the truth table for the NAND and NOR gates




A	B	x
0	0	
0	1	
1	0	
1	1	

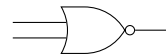

A	B	x
0	0	
0	1	
1	0	
1	1	

2. For the following logic circuit

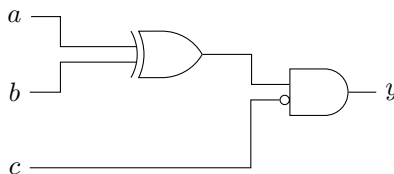

- (a) **[3 points]** Complete the truth table for all 3 bit inputs for a, b, c and output y

a	b	c	y

- (b) **[2 points]** Write the boolean equation for this circuit.

3. [5 points] Draw a circuit for the following formula

$$f = \overline{(A + B) \cdot C} + D$$

4. [5 points] Show the sum of products for the following truth table

a	b	c	f
0	0	0	1
0	1	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	1	1	1
1	1	0	0
1	1	1	0

5. Simplify the following equations (use Boolean laws)


(a) [1 point] $B(A + 0)$

(b) [1 point] $B(A\overline{A})$

(c) [1 point] $(A + \overline{B})(\overline{A} + B)$

(d) [2 points] $\overline{(A + B)} \cdot (A + B + C)$

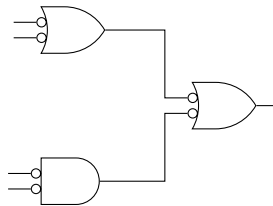6. [5 points] Use bubble pushing to simplify this circuit



7. Using the following truth table

a	b	c	f
0	0	0	0
0	1	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	1	1	1
1	1	0	1
1	1	1	1

(a) **[5 points]** Show the sum of products.

(b) **[5 points]** Simplify the above equation.

8. Simplify the following equations

(a) **[2 points]** $C(A + 1)$

(b) **[2 points]** $AB(A + C)$

(c) **[2 points]** $(A + \overline{B})(\overline{A} + c)$

(d) **[2 points]** $(B + 0)(C + D + 1)$

9. Using the following truth table

a	b	c	f
0	0	0	1
0	1	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	1	1	0
1	1	0	1
1	1	1	0

(a) **[3 points]** Fill in the following K-Map

	$\bar{b}\bar{c}$	$\bar{b}c$	bc	$b\bar{c}$
a				
\bar{a}				

(b) **[2 points]** Minimize the function using the K-map

(c) **[5 points]** Draw the two-level circuit for this function

10. [5 points] Suppose we already have this k-Map.

	\overline{CD}	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1	0	0	1
$\overline{A}B$	1	1	1	1
AB	1	1	0	0
$A\overline{B}$	0	0	0	1

Minimize the function

11. Consider your answer to question 9.c, the particular two-level, minimal circuit.

(a) [1 point] Is your answer unique? In other words, is there only one possible two-level circuit for that K-Map that is minimal, or is there another one that is logically different but still correct and just as small? (**Answer either UNIQUE or NOT UNIQUE**)

(b) [3 points] Will this always be the case, or could a different K-map change your answer?

12. [10 points] Suppose we already have this K-map. Minimize the function.

	\overline{CD}	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1	0	1	1
$\overline{A}B$	0	1	1	1
AB	1	1	1	0
$A\overline{B}$	1	0	1	1

13. [10 points] Suppose we already have this K-map. Minimize the function.

	\overline{CD}	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	0	X	0	0
$\overline{A}B$	1	1	1	1
AB	0	1	0	X
$A\overline{B}$	0	X	0	0